

## Chapter 13: Basic Op-Amp Circuits

■ In the last chapter, you learned about the principles, operation, and characteristics of the operational amplifier.

■ Op-amps are used in such a wide variety of circuits and applications that it is impossible to cover all of them in one chapter, or even in one book. Therefore, in this chapter, four fundamentally important circuits are covered to give you a foundation in op-amp circuits.

■ The basic circuits for op-amp's are

- 1- Comparators
- 2- Summing Amplifiers
- 3- Integrators and Differentiators

### 13.1: Comparators

■ A **comparator** is a specialized *nonlinear* op-amp circuit that compares between two input voltages and produces an output state that indicates which one is greater. Comparators are designed to be fast and frequently have other capabilities to optimize the comparison function.


■ In this application, the op-amp is used in the open-loop configuration, with the input voltage on one input and a reference voltage on the other.

### 13.1: Comparators

■ One application of an op-amp used as a comparator is to determine when an input voltage exceeds a certain level
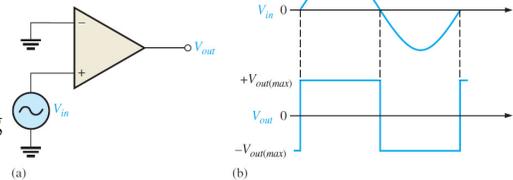
#### Zero-Level Detection

■ The figure shown is the zero-level detector circuit; the inverting (-) input is grounded to produce a zero level (reference to compare with), and the input signal voltage is applied to the noninverting (+) input



■ Since  $V_{in}$  is at noninverting input As shown in figure;

→ Any  $V_{in}$  above the zero will produce a +ve saturated output ( $+V_{out(max)}$ )


→ any  $V_{in}$  below the zero will produce a -ve saturated output ( $-V_{out(min)}$ )

■ Saturation of the output is due to the open-loop op-amp that have a very high voltage gain → very small difference voltage between the two inputs drives the amplifier into saturation (non linear operation)

### 13.1: Comparators
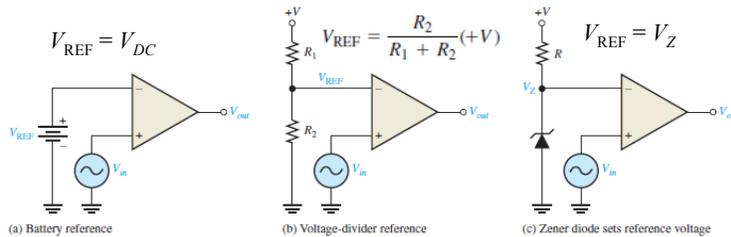
#### Nonzero-Level Detection


■ The reference voltage can be set to non zero voltage (+ve or -ve) by adding a dc voltage or voltage divider or zener or ....



■ As shown in the output voltage for given input (sinewave)

→ Any voltage above  $V_{REF} \rightarrow V_{out}$  will be saturated +ve ( $V_{out(max)}$ )

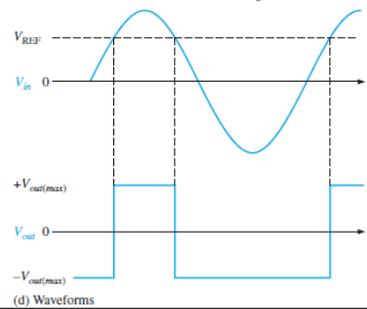→ Any voltage Below  $V_{REF} \rightarrow V_{out}$  will be saturated -ve ( $V_{out(min)}$ )



### 13.1: Comparators




#### Nonzero-Level Detection: Example

For the given comparator and input signal, draw the output showing its proper relationship to the input signal. Assume the maximum output levels of the comparator are ;  $\pm 14$  V.

$$V_{REF} = \frac{R_2}{R_1 + R_2} (+V)$$

$$= \frac{1.0 \text{ k}\Omega}{8.2 \text{ k}\Omega + 1.0 \text{ k}\Omega} (+15 \text{ V})$$

$$= 1.63 \text{ V}$$

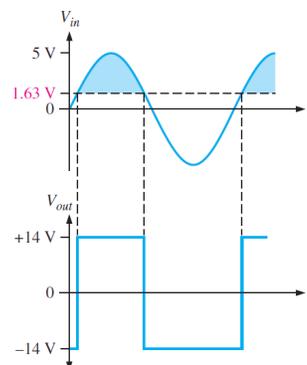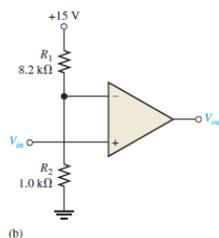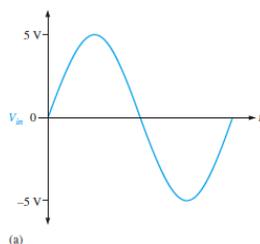


### 13.1: Comparators
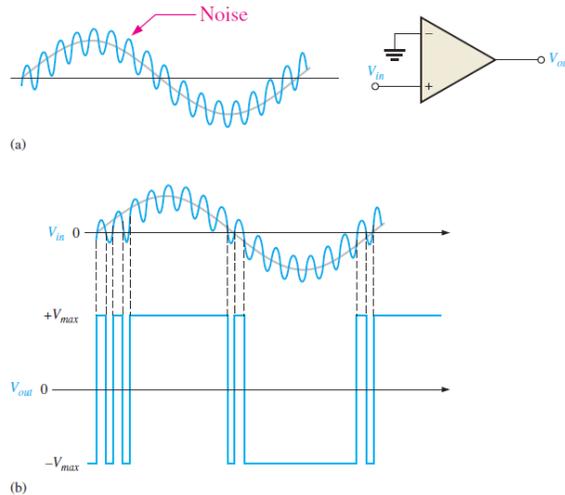
#### Effects of Input Noise on Comparator Operation

In many practical situations, noise (unwanted voltage fluctuations) appears (superimposed) on the input line → we will have an erratic (شاذ) output voltage

- When the sine wave approaches 0, the fluctuations due to noise may cause the total input to vary above and below 0 several times, thus producing an erratic output voltage as shown



### 13.1: Comparators


#### Reducing Noise Effects with Hysteresis

- **Hysteresis** is incorporated by adding regenerative (positive) feedback, which creates two switching points: the upper trigger point (UTP) and the lower trigger point (LTP). After one trigger point is crossed, it becomes inactive and the other one becomes active.

When  $V_{out}$  is  $+V_{out(max)}$  → UTP is set by

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)})$$

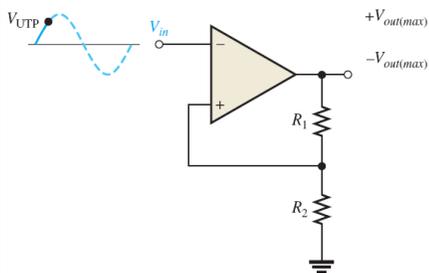
→ When  $V_{in}$  exceeds UTP, the output switches to the  $-V_{out(max)}$



When  $V_{out}$  is  $-V_{out(max)}$  → LTP is set by

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)})$$

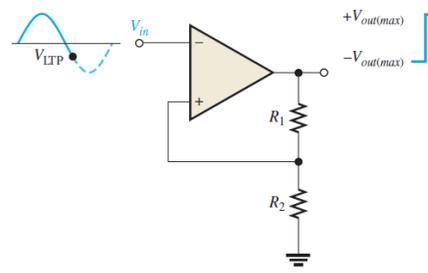→ When  $V_{in}$  goes below LTP, the output switches to the  $+V_{out(max)}$



### 13.1: Comparators


#### Reducing Noise Effects with Hysteresis

■ Hence, the device triggers only once when UTP or LTP is reached as shown; thus, there is immunity to noise that is riding on the input signal.

■ The amount of hysteresis is defined by the difference of the two trigger levels.

$$V_{HYS} = V_{UTP} - V_{LTP}$$

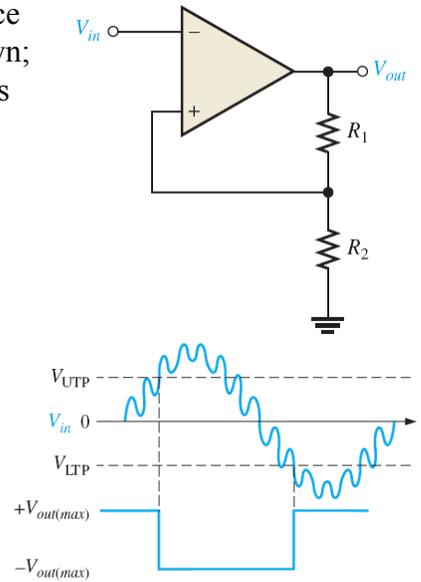
■ A comparator with built-in hysteresis is sometimes known as a **Schmitt trigger**.



### 13.1: Comparators
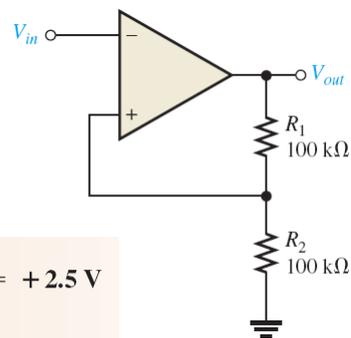
#### Reducing Noise Effects with Hysteresis: Example

Determine the upper and lower trigger points for the comparator circuit in figure. Assume that  $+V_{out(max)} = +5\text{ V}$  and  $-V_{out(max)} = -5\text{ V}$ .




$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)}) = 0.5(5\text{ V}) = +2.5\text{ V}$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)}) = 0.5(-5\text{ V}) = -2.5\text{ V}$$
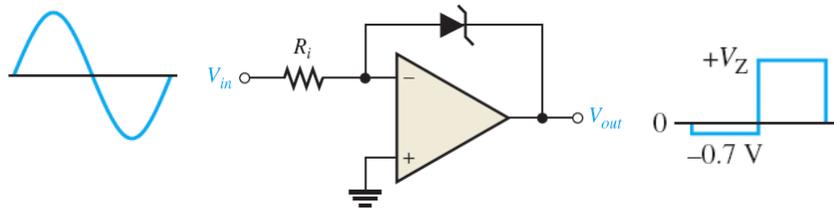
### 13.1: Comparators Output Bounding


- In some applications, it is necessary to limit the output voltage levels of a comparator to a value less than that provided by the saturated op-amp.
- A process of limiting the output called **bounding** can be used by adding a single zener diode to limit the output voltage to the zener voltage in one direction and to the forward diode voltage drop in the other direction.

- If zener anode is connected to inverting input (virtual ground,  $V = 0$ )  $\rightarrow$  when  $V_{out}$  is +ve, zener is reverse  $\rightarrow V_{out} = +V_Z$
- $\rightarrow$  When  $V_{out}$  is -ve, zener is forward  $\rightarrow V_{out} = -0.7V$
- $\rightarrow$  positive bounded output



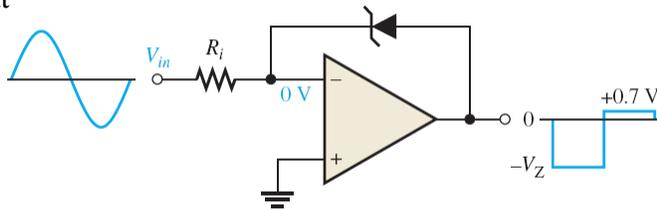
### 13.1: Comparators Output Bounding

- If zener is reversed, the result will be the inverse  $\rightarrow$  negative bounded out put



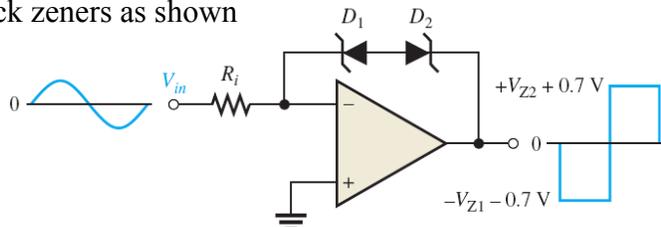- Positive and negative bounded out put can be obtained by putting two back to back zeners as shown



### 13.1: Comparators

#### Output Bounding: Example

Determine the output voltage waveform

We have zener diodes between input and output  $\rightarrow$  Bounded output.

But we have feedback to (+) op-amp input  $\rightarrow$  we have also hysteresis voltages

Since input voltage is at inverting (-) input  $\rightarrow V$  at (-) =  $V$  at (+) = hysteresis voltage  $\rightarrow$  Hence  $V_{out}$  will be  $V_{zeners} + V_{hysterisi}$

At +ve  $V_{out} \rightarrow +V_{out} = V_{UPT} + V_{z2} + 0.7 = V_{UPT} + 5.4$



$$\text{But } V_{UPT} = \frac{R_2}{R_2 + R_1} (+V_{out}) = \frac{47}{147} (+V_{out}) = 0.32(+V_{out})$$

$$\rightarrow +V_{out} = 0.32(+V_{out}) + 5.4$$

$$\rightarrow +V_{out} = 7.94V$$

Same can be found when  $V_{out}$  is -ve

$$\rightarrow -V_{out} = -7.94V$$

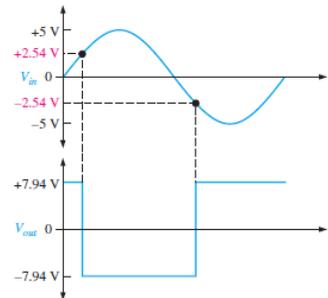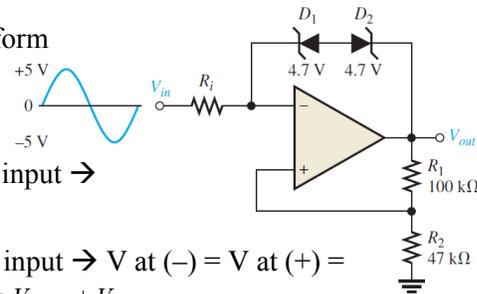

### 13.1: Comparators


#### Comparator Applications

#### Over-Temperature Sensing Circuit

■ For the shown bridge,  $R_3 = R_4$  and  $R_1$  is high ( $> R_2$ ) at normal temperatures  $\rightarrow V$  at (+) is lower than  $V$  at (-).

■ As the temperature increases, the resistance of the thermistor ( $R_1$ ) decreases  $\rightarrow V$  at (+) input increase.

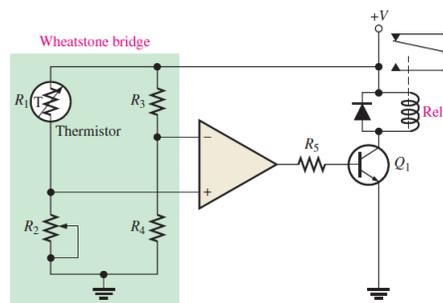When the temperature reaches the critical value,  $R_1$  becomes equal to  $R_2$ , and the bridge becomes balanced (since  $R_3 = R_4$ ). At this point the op-amp  $V_{out}$  switches from low to its high saturated output level, turning  $Q_1$  on. This energizes the relay, which can be used to activate an alarm or initiate an appropriate response to the over-temperature condition.




### 13.1: Comparators

#### Comparator Applications
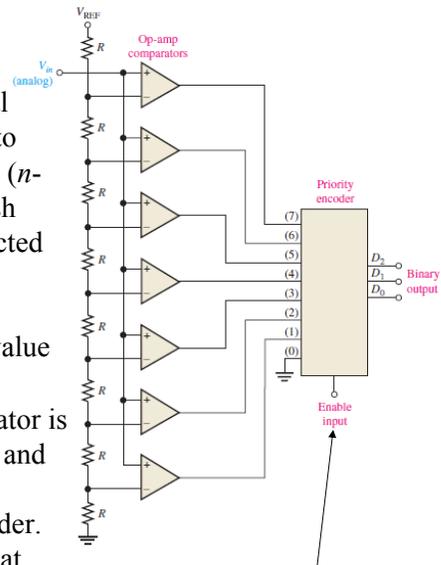
#### Analog-to-Digital (A/D) Conversion

■ Simultaneous or flash analog-to-digital converters (ADC) use  $2^n-1$  comparators to convert an analog input to a digital value ( $n$ -digit binary number) for processing. Flash ADCs are a group of comparators connected in parallel, each with a slightly different reference voltage. The priority encoder produces an output equal to the highest value input.



■ The reference voltage for each comparator is set by the resistive voltage divider circuit and  $V_{REF}$ . The output of each comparator is connected to an input of the priority encoder. The *priority encoder* is a digital device that produces a binary number on its output representing the highest value input.



The encoder samples its input when a pulse occurs on the enable line (sampling pulse)
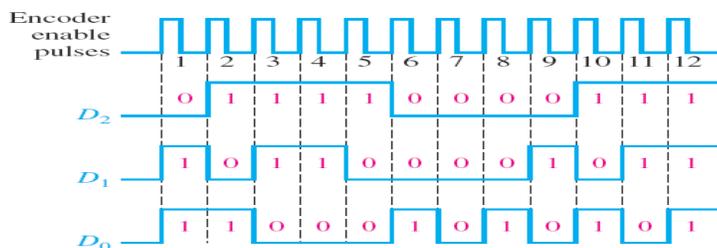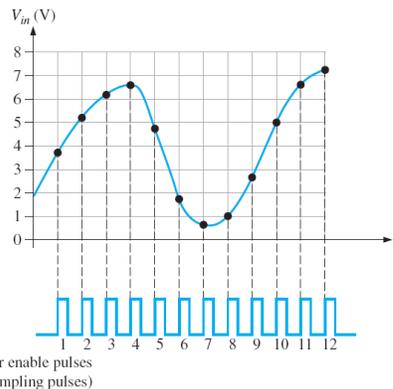
### 13.1: Comparators

for the input signal in Figure below  
 Determine the binary number sequence of the three-digit simultaneous ADC (Figure shown before). Draw the resulting digital output waveforms.  $V_{REF} = +8V$



Digital numbers: **011, 101, 110, 110, 100, 001, 000, 001, 010, 101, 110, 111**

### 13.2: Summing Amplifiers

■ The summing amplifier is an application of the inverting op-amp covered in Chapter 12. The averaging amplifier and the scaling amplifier are variations of the basic summing amplifier.


#### Summing Amplifier with Unity Gain

■ A **summing amplifier** has two or more inputs; normally all inputs have unity gain. The output is proportional to the negative of the algebraic sum of the inputs.

$$I_T = I_1 + I_2 \quad \text{Since } V_{OUT} = -I_T R_f$$

$$\rightarrow V_{OUT} = -(I_1 + I_2)R_f$$
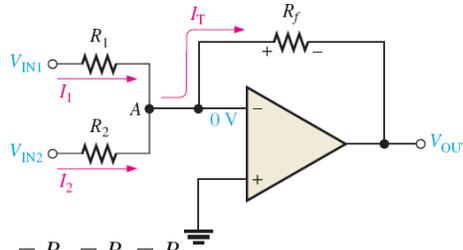
$$= -\left(\frac{V_{IN1}}{R_1} + \frac{V_{IN2}}{R_2}\right)R_f$$



For unity gain inverting amplifier  $\rightarrow R_1 = R_2 = R_f = R$


$$V_{OUT} = -\left(\frac{V_{IN1}}{R} + \frac{V_{IN2}}{R}\right)R = -(V_{IN1} + V_{IN2})$$

In general, for n inputs  $\rightarrow V_{OUT} = -(V_{IN1} + V_{IN2} + V_{IN3} + \dots + V_{INn})$

### 13.2: Summing Amplifiers

#### Summing Amplifier with Unity Gain: Example

Determine the output voltage in Figure

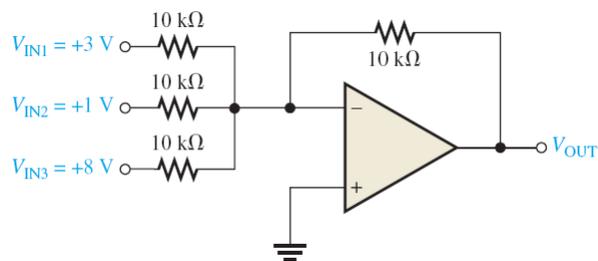

$$V_{OUT} = -(V_{IN1} + V_{IN2} + V_{IN3}) = -(3 \text{ V} + 1 \text{ V} + 8 \text{ V}) = -12 \text{ V}$$


## 13.2: Summing Amplifiers

### Summing Amplifier with Gain Greater Than Unity

■ When  $R_f$  is larger than the input resistors, the amplifier has a gain of  $R_f/R$ , where  $R$  is the value of each equal-value input resistor. The general expression for the output is

$$V_{OUT} = -\frac{R_f}{R}(V_{IN1} + V_{IN2} + \dots + V_{INn})$$

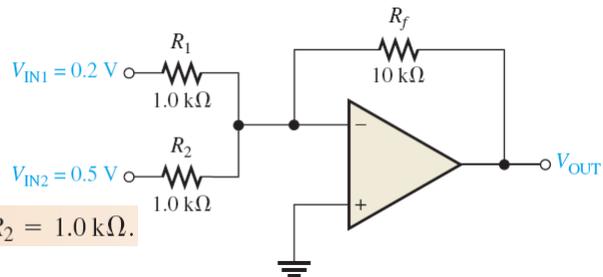**Example:** Determine the output voltage for the summing amplifier shown



$R_f = 10 \text{ k}\Omega$  and  $R = R_1 = R_2 = 1.0 \text{ k}\Omega$ .


$$\rightarrow V_{OUT} = -\frac{R_f}{R}(V_{IN1} + V_{IN2}) = -\frac{10 \text{ k}\Omega}{1.0 \text{ k}\Omega}(0.2 \text{ V} + 0.5 \text{ V}) = -10(0.7 \text{ V}) = -7 \text{ V}$$

## 13.2: Summing Amplifiers

### Averaging Amplifier

■ An **averaging amplifier** is basically a summing amplifier with the gain set to  $R_f/R = 1/n$  ( $n$  is the number of inputs). The output is the negative average of the inputs.

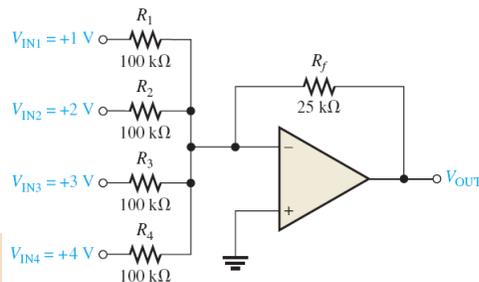**Example:** Show that the amplifier in Figure produces an output whose magnitude is the mathematical average of the input voltages.



$$\begin{aligned} V_{OUT} &= -\frac{R_f}{R}(V_{IN1} + V_{IN2} + V_{IN3} + V_{IN4}) \\ &= -\frac{25 \text{ k}\Omega}{100 \text{ k}\Omega}(1 \text{ V} + 2 \text{ V} + 3 \text{ V} + 4 \text{ V}) = -\frac{1}{4}(10 \text{ V}) = -2.5 \text{ V} \end{aligned}$$

$$V_{IN(\text{avg})} = \frac{1 \text{ V} + 2 \text{ V} + 3 \text{ V} + 4 \text{ V}}{4} = \frac{10 \text{ V}}{4} = 2.5 \text{ V}$$

### 13.2: Summing Amplifiers

#### Scaling Adder

■ A **scaling adder** has two or more inputs with each input having a different gain. The output represents the negative *scaled* sum of the inputs. the output voltage


$$\text{can be expressed as } V_{\text{OUT}} = -\left(\frac{R_f}{R_1}V_{\text{IN1}} + \frac{R_f}{R_2}V_{\text{IN2}} + \cdots + \frac{R_f}{R_n}V_{\text{INn}}\right)$$

**Example:** Determine the weight of each input voltage for the scaling adder in Figure and find the output voltage.

$$\text{Weight of input 1: } \frac{R_f}{R_1} = \frac{10 \text{ k}\Omega}{47 \text{ k}\Omega} = \mathbf{0.213}$$

$$\text{Weight of input 2: } \frac{R_f}{R_2} = \frac{10 \text{ k}\Omega}{100 \text{ k}\Omega} = \mathbf{0.100}$$
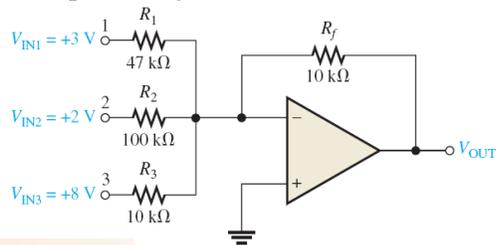
$$\text{Weight of input 3: } \frac{R_f}{R_3} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega} = \mathbf{1.00}$$



$$\begin{aligned} V_{\text{OUT}} &= -\left(\frac{R_f}{R_1}V_{\text{IN1}} + \frac{R_f}{R_2}V_{\text{IN2}} + \frac{R_f}{R_3}V_{\text{IN3}}\right) \\ &= -[0.213(3 \text{ V}) + 0.100(2 \text{ V}) + 1.00(8 \text{ V})] \\ &= -(0.639 \text{ V} + 0.2 \text{ V} + 8 \text{ V}) = \mathbf{-8.84 \text{ V}} \end{aligned}$$


### 13.2: Summing Amplifiers

#### Applications: Digital to analogue convertor (DAC)

■ An application of a **scaling adder** is the D/A converter circuit shown here. the method shown here is useful only for small DACs.

■ The resistors are inversely proportional to the binary column weights (The lowest-value resistor  $R$  corresponds to the highest weighted binary input ( $2^3$ ). All of the other resistors are multiples of  $R$  and correspond to the binary weights  $2^2$ ,  $2^1$ , and  $2^0$ ).

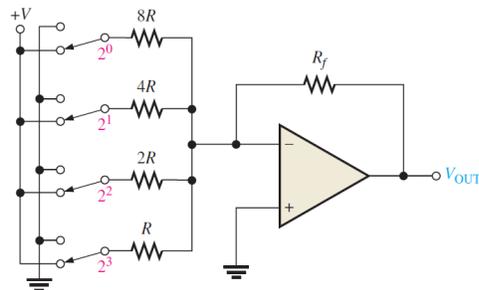
■ The inverting input is at virtual ground, and so the output voltage is proportional to the current through the feedback resistor  $R_f$  (sum of input currents)  $\rightarrow V_{\text{out}} = -IR_f$



### 13.2: Summing Amplifiers
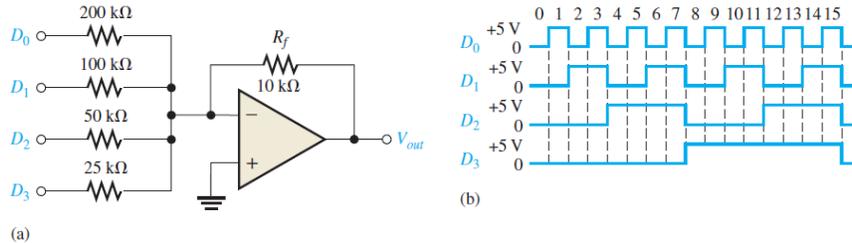
#### Applications: Digital to analogue convertor (DAC): Example

Determine the output voltage of the DAC for the four digit sequence binary codes shown, that are applied to the inputs. A high level is a binary 1, and a low level is a binary 0. The least significant binary digit is  $D_0$ .



For each input digit, we can calculate the current when it is at high (1) level at +5V

$$I_0 = \frac{5\text{ V}}{200\text{ k}\Omega} = 0.025\text{ mA} \quad I_1 = \frac{5\text{ V}}{100\text{ k}\Omega} = 0.05\text{ mA} \quad I_2 = \frac{5\text{ V}}{50\text{ k}\Omega} = 0.1\text{ mA} \quad I_3 = \frac{5\text{ V}}{25\text{ k}\Omega} = 0.2\text{ mA}$$

For each input digit, we have a corresponding digit output voltage

$$V_{\text{OUT}(D_0)} = -R_f I_0 = -(10\text{ k}\Omega)(0.025\text{ mA}) = -0.25\text{ V} \quad V_{\text{OUT}(D_2)} = -R_f I_2 = -(10\text{ k}\Omega)(0.1\text{ mA}) = -1\text{ V}$$

$$V_{\text{OUT}(D_1)} = -R_f I_1 = -(10\text{ k}\Omega)(0.05\text{ mA}) = -0.5\text{ V} \quad V_{\text{OUT}(D_3)} = -R_f I_3 = -(10\text{ k}\Omega)(0.2\text{ mA}) = -2\text{ V}$$

### 13.2: Summing Amplifiers


#### Applications: Digital to analogue convertor (DAC):

#### Example – continued from previous

■ Hence for any given digital value, the output will be the sum of corresponding digit output voltage:

input	Addition of digit voltages	Total ( $V_{\text{out}}$ )
0000	0-0-0-0	0
0001	0-0-0-0.25	-0.25
0010	0-0-0.5-0	-0.5
0011	0-0-0.5-0.25	-0.75
0100	0-1-0-0	-1
0101	0-1-0-0.25	-1.25
0110	0-1-0.5-0	-1.5
⋮	⋮	⋮
1111	2-1-0.5-0.25	-3.75

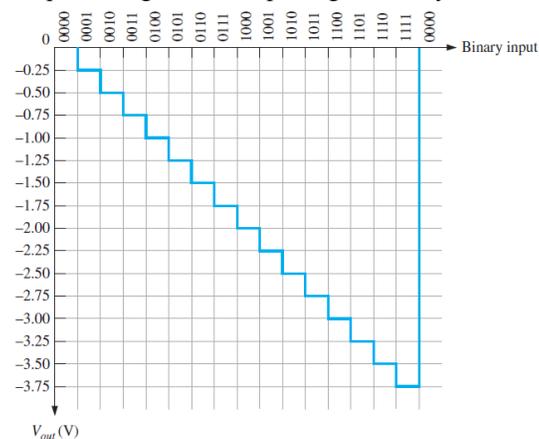Output voltage versus input digital binary data




### 13.2: Summing Amplifiers

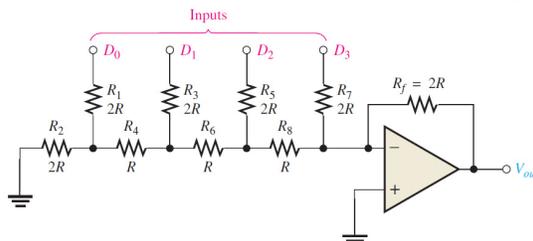
#### Applications: Digital to analogue convertor (DAC):

■ A more widely used method for D/A conversion is the **R/2R ladder**. The gain for  $D_3$  is  $-1$ . Each successive input has a gain that is half of previous one. The output represents a weighted sum of all of the inputs (similar to the scaling adder).

→ the output voltage is proportional to the binary weight of the input bits



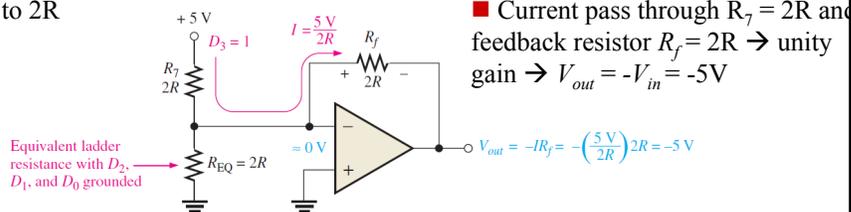With  $D_3 = 1$  (+5V) and  $D_2 = 0, D_1 = 0, D_0 = 0$  → For circuit before  $D_3$  input (before  $R_7$ ) → the equivalent resistor can be calculated to be equal to  $2R$




### 13.2: Summing Amplifiers
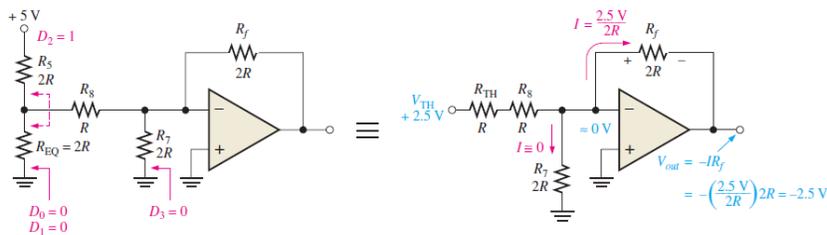
#### Applications: Digital to analogue convertor (DAC):

■ With  $D_2 = +V$  → if we thevinize the circuit before  $R_8$  → we will have  $R_{TH} = R$  and  $V_{TH} = +2.5$  ( $= +5/2$ ). Again with unity gain →  $V_{out} = -V_{in} = -V_{TH} = -2.5V$  → gain for  $D_2 = 1/2$  gain for  $D_3$

→ With  $D_2 = 1$  (+5V) and  $D_3 = 0, D_1 = 0, D_0 = 0$  →  $V_{out} = -2.5$



(b) Equivalent circuit for  $D_3 = 0, D_2 = 1, D_1 = 0, D_0 = 0$

This process is repeated for other inputs

→ With  $D_1 = 1$  (+5V) and  $D_3 = 0, D_2 = 0, D_0 = 0$  →  $V_{out} = -1.25 V$

→ With  $D_0 = 1$  (+5V) and  $D_3 = 0, D_2 = 0, D_1 = 0$  →  $V_{out} = -0.625 V$

■ Hence, for different digital data input → The output represents a weighted sum of all of the inputs (similar to the scaling adder).

### 13.3: Integrators and differentiators

An op-amp **integrator** simulates mathematical integration, and **differentiator** simulates mathematical differentiation.

#### The Op-Amp Integrator: Ideal integrator

■ The **ideal integrator** is an inverting amplifier that has a capacitor in the feedback path. The output voltage is proportional to the negative integral (running sum) of the input voltage.

For capacitor  $Q = I_C t$  (current charge relation)

Also charge on capacitor is


$$Q = CV_C \longrightarrow V_C = \left(\frac{I_C}{C}\right)t$$

Since  $V_{in}$  is constant  $\rightarrow I_i = V_{in}/R_i = I_C$  is constant

Hence  $I_C/C$  is constant  $\rightarrow V_C = \left(\frac{I_C}{C}\right)t$  is an equation of a straight line with a constant slope  $I_C/C$ .

$V_{out} = -V_C$ , because (-) input of op-amp is virtual ground  $\rightarrow V_{out} = -\left(\frac{I_C}{C}\right)t$

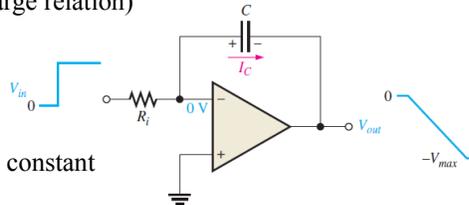$\rightarrow$  output change or slope of the integrator  $\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{R_i C}$



### 13.3: Integrators and differentiators

#### The Op-Amp Integrator: Ideal integrator

■ As you can see the output voltage is the time integral of input voltage as also shown below

$dq = Idt$ , But also  $dq = CdV$


$\rightarrow CdV_C = I_C dt$ , Integrate both sides

$$\rightarrow \int CdV_C = \int I_C dt$$

But  $I_C = I_i = V_{in} / R_i$

$$\int CdV_C = \int \frac{V_{in}}{R_i} dt$$

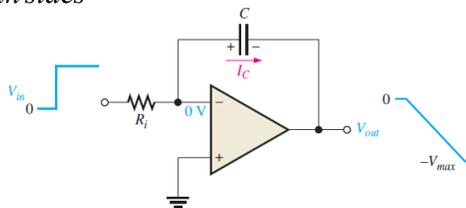$\Rightarrow \Delta V_{out} = -\frac{V_{in}}{R_i C} \Delta t$  (-ve sign is added for inverting output)



### 13.3: Integrators and differentiators


#### The Op-Amp Integrator: Ideal integrator -Example

(a) Determine the rate of change of the output voltage in response to the input square wave, as shown for the ideal integrator in Figure The output voltage is initially zero. The pulse width is  $200\mu\text{s}$

(b) Describe the output and draw the waveform.

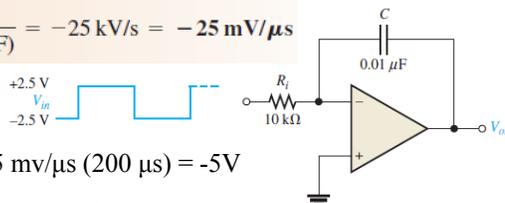(a) When (a) in is +ve (+2.5 V)

$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{R_f C} = -\frac{2.5 \text{ V}}{(10 \text{ k}\Omega)(0.01 \mu\text{F})} = -25 \text{ kV/s} = -25 \text{ mV}/\mu\text{s}$$




→ For  $200 \mu\text{s}$  width,  $\Delta V_{out} = -25 \text{ mV}/\mu\text{s} (200 \mu\text{s}) = -5\text{V}$

When (a) in is -ve (-2.5 V)

$$\frac{\Delta V_{out}}{\Delta t} = +\frac{V_{in}}{R_f C} = +25 \text{ mV}/\mu\text{s}$$

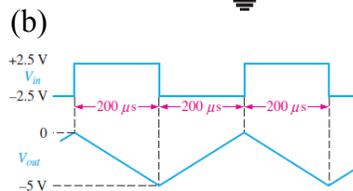$\Delta V_{out} = -25 \text{ mV}/\mu\text{s} (200 \mu\text{s}) = 5\text{V}$



### 13.3: Integrators and differentiators


#### The Op-Amp Integrator: Practical integrator

■ Op-amp integrating circuits must have extremely low dc offset and bias currents, because small errors are equivalent to a dc input. The ideal integrator tends to accumulate these errors, which moves the output toward saturation (high infinite open loop gain because C is open to dc).

■ The **practical integrator** overcomes these errors– the simplest method is to add a relatively large feedback resistor  $R_f$  → Relatively very small error compared to integrator without  $R_f$ .

■ Also we may add  $R_c$  to (+) input to balance the effect of bias current

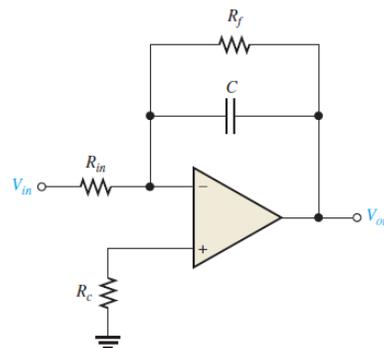■ Calculations will be same as for ideal integrators




### 13.3: Integrators and differentiators

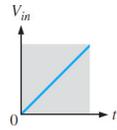
#### The Op-Amp Differentiator

■ The **ideal differentiator** is an inverting amplifier that has a capacitor in the input path. The output voltage is proportional to the negative rate of change of the input voltage.

In this case,  $V_{in} = V_C$  is linearly increase with time  
From basic capacitor relation  $\rightarrow$


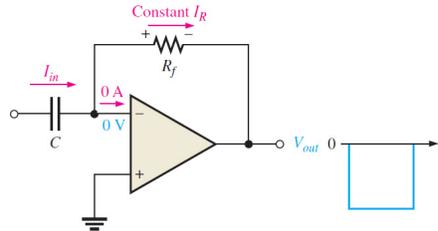
$$V_C = (I_C/C)t \quad \rightarrow \quad I_C = \left(\frac{V_C}{t}\right)C$$



The output voltage is  $V_{out} = -I_R R_f = -I_C R_f$  Because I through the op-amp = 0


$$\rightarrow V_{out} = -\left(\frac{V_C}{t}\right)R_f C \quad \text{Which is constant (as shown) because the slope} = dV_{in}/dt = V_C/t = V_{in}/C \text{ is constant}$$

Note that  $R_f C$  is the  $RC$  circuit time constant

### 13.3: Integrators and differentiators
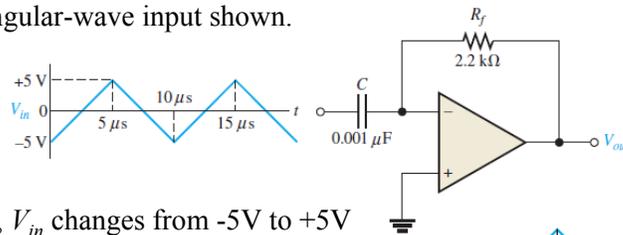
#### The Op-Amp Differentiator: Ideal differentiator - Example

Determine the output voltage of the ideal op-amp differentiator in Figure for the triangular-wave input shown.




In  $5\mu s$ ,  $V_{in}$  changes from  $-5V$  to  $+5V$

$$\rightarrow \text{slope} \quad \frac{V_C}{t} = \frac{10V}{5\mu s} = 2V/\mu s$$

The time constant is

$$R_f C = (2.2k\Omega)(0.001\mu F) = 2.2\mu s$$
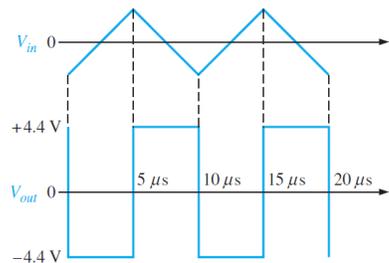
$$\rightarrow V_{out} = -\left(\frac{V_C}{t}\right)R_f C = -(2V/\mu s)2.2\mu s = -4.4V$$



For the  $-ve$  slope input voltage  $\rightarrow V_{out} = +4.4V$

### 13.3: Integrators and differentiators

#### The Op-Amp Differentiator: Practical differentiator

The very low reactance of  $C$  at high frequencies means an ideal differentiator circuit has very high gain for high-frequency noise. To compensate for this, a small series resistor is often added to the input. This **practical differentiator** has reduced high frequency gain and is less prone to noise.

■ Also we may add  $R_c$  to (+) input to balance the effect of bias current

■ Calculations will be same as for ideal differentiator

